

## **SYLLABUS**

1. Implementation of Logic Gates –Data flow model and Behavioral model
2. Combinational logic circuits –Adders and Subtractor
3. Code converters-Binary to Gray and Gray to Binary
4. 3 to 8 Decoder –74138
5. 4 Bit Comparator –7485
6. 8 x 1 Multiplexer –74151 and 2X4 Demultiplexer –74155
7. 16 x 1 Multiplexer –74150 and 4X16 Demultiplexer –74154
8. Sequential circuits -Flip-Flops
9. Decade counter –7490.
10. Synchronous & Asynchronous Counters
11. Shift registers –7495.
12. Universal shift registers –74194/195.
13. RAM (16 x 4) –74189 (Read and Write operations).
14. Stack and Queue Implementation using RAM.

EX.NO:1

DATE:

## Design Logic Gates Using Verilog HDL in Xilinx Platform

### Aim:

To develop the source code for logic gates by using VERILOG and obtain the simulation.

### Software Required:

- Xilinx – Project Navigator
- ModelSim Simulator

### Procedure:

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using source code.

Step3: Write the source code in VERILOG.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.


Step5: Verify the output by simulating the source code.

### Logic Diagram:

#### AND Gate:

Logic Diagram:  
Table

Truth Table:

 


A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

#### OR Gate:

Logic diagram

Truth

 


A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

#### NOT Gate:

Logic Diagram:  
Table

Truth Table:

 

A	Y=A'
0	1
1	0

#### NAND Gate:

Logic Diagram

Truth




A	B	Y=(ab)'
0	0	1
0	1	1
1	0	1
1	1	0

#### NOR Gate:

Logic Diagram:

Truth Table:

 


A	B	Y=(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

#### XOR Gate:

Logic Diagram


Truth Table

 

A	B	Y=A⊕B
0	0	0
0	1	1
1	0	1
1	1	0

#### XNOR Gate:

Logic diagram:

 

Truth table:

A	B	Y=A⊙B
0	0	1
0	1	0
1	0	0
1	1	1

**Verilog Code:****AND Gate:**

```
module andgate(a,b, c);  
input a,b;  
output c;  
assign c=a & b;  
endmodule
```

**Simulation Output:****OR Gate:**

```
module orgate(a,b, c);  
input a,b;  
output c;  
assign c= a |b;  
endmodule
```

**Simulation Output:****NOT Gate:**

```
module notgate(a, abar);  
input a;  
output abar;  
assign abar = ~a;  
endmodule
```

**Simulation Output:****NAND Gate:**

```
module nandgate(a,b, c);  
input a,b;  
output c;  
assign c = ~(a & b);  
endmodule
```

**Simulation output:****NOR Gate:**

```
module norgate(a,b, c);  
input a,b;  
output c;  
assign c = ~(a | b);  
endmodule
```

**Simulation Output:****XOR Gate:**

```
module exorgate(a,b, c);  
input a,b;  
output c;  
assign c = a ^ b;  
endmodule
```

**Simulation Output:****XNOR Gate:**

```
module exnorgate(a,b, c);  
input a,b;  
output c;  
assign c = ~(a ^ b);  
endmodule
```

**Simulation Output:****Result:**

Thus the gates (AND, OR, NOT, NAND, NOR, XOR and XNOR gates) are simulated verified with VERILOG program.

**EX.NO:2**

**DATE:**

**BASIC EXPERIMENTS**

**Aim:**

To Simulate and synthesis Adders and subtractors using Verilog HDL

**Software tools required:**

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

**a) Half Adder and Half subtractors.**

**ALGORITHM:**

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using VERILOG source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.


**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

**HALF ADDER:**

**LOGIC DIAGRAM:**

 

**TRUTH TABLE:**


A	B	SUM (s)	CARRY (ca)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**VERILOG CODING:**


**Dataflow Modeling:**

```
module ha_dataflow(a, b, s, ca);
    input a;
    input b;
    output s;
    output ca;
    assign#2 s=a^b;
    assign#2 ca=a&b;
endmodule
```

### Simulation output:

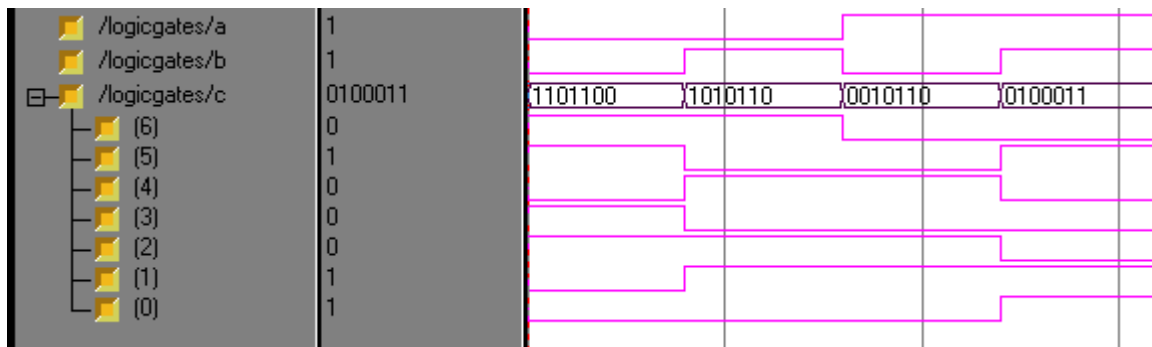


### Synthesis RTL Schematic:

 

### HALF SUBTRACTOR:

#### LOGIC DIAGRAM:

 

#### TRUTH TABLE:

A	B	DIFFERENCE (diff)	BORROW (bor)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### VERILOG CODING:

#### Dataflow Modeling:

```
module hs_dataflow(a, b, dif, bor);
    input a;
    input b;
    output dif;
    output bor;
    wire s1;
    assign#3 abar=~a;
    assign#3 dif=a^b;
    assign#3 bor=b&s1;
endmodule
```


## HALF SUBTRACTOR:

### Synthesis RTL Schematic:

### Simulation output:



### Synthesis RTL Schematic:

 

## b) Full Adder and Full Subtractors.

### Aim:

To Simulate and synthesis Full Adders and Full subtractors using Verilog HDL

### Software tools required:

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

### ALGORITHM:

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using Verilog source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.


**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

## FULL ADDER:

### LOGICDIAGRAM:

 


### TRUTH TABLE:

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### Dataflow Modeling:

```
module fulsubdataflow(a, b, cin, sum, carry);
  input a;
  input b;
  input cin;
  output sum;
  output carry;
  wire s1,d1,d2;
  assign s1= a^b;
  assign diff=s1^cin;
  assign d1= a and b;
  assign d2= s1 and cin;
  assign carry=(d1 | d2);
endmodule
```
 
### Structural Modeling Full Adder using Half Adder:




```
module fa_2ha(a, b, cin, sum, carry);
  input a;
  input b;
  input cin;
  output sum;
  output carry;
  wire p,q,r;
  ha_dataflow
  h1(a,b,p,q),
  h2(p,cin,sum,r),
  or2(q,r,carry);
endmodule
```

```

        h2(p,cin,sum,r);
        or o1(carry,q,r);
    endmodule
Dataflow Modeling
    module ha_dataflow(a, b, sum, carry);
        input a;
        input b;
        output sum;
        output carry;
        assign#3 sum=a^b;
        assign#3 carry=a&b;
    endmodule


```

### **Simulation output:**

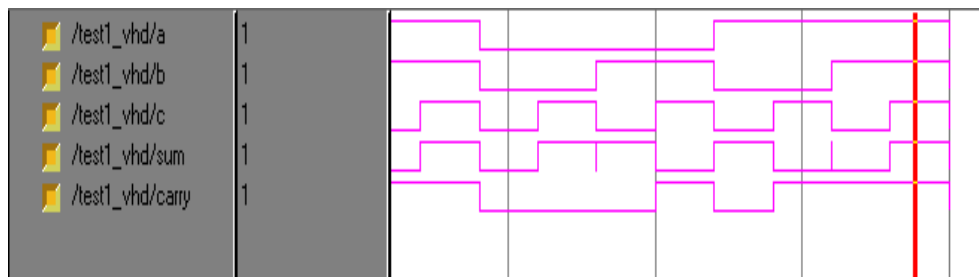

### **FULL SUBTRACTOR:**

#### **LOGIC DIAGRAM:**

 

#### **TRUTH TABLE:**

A	B	C	DIFFERENCE	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

#### **Dataflow Modeling:**

```

    module fulsubdataflow(a, b, c, diff, borrow);
        input a;
        input b;
        input c;
        output diff;
        output borrow;
        wire s1,s2,s3,s4,s5;
        assign s1= a^b;
        assign diff=s1^cin;
        assign s2= ~a;
        assign s3= s2 and b;
        assign s4= b and c;
        assign s5=s2 and c;
        assign borrow=(s3 | (s4) s5);
    endmodule

```




### Structural Modeling:

```
module fs_2hs(a, b, c, diff, borrow);
  input a;
  input b;
  input c;
  output diff;
  output borrow;
  wire p,q,r;
  hs_dataflow
    h1(a,b,p,q),
    h2(p,c,diff,r);
  or o1(borrow,q,r);
endmodule
```

### Dataflow Modeling


```
module hs_dataflow(a, b, dif, bor);
  input a;
  input b;
  output dif;
  output bor;
  wire abar;
  assign#3 abar=~a;
  assign#3 dif=a^b;
  assign#3 bor=b&abar;
endmodule
```

### Simulation output:

 


### FULL ADDER:

#### Synthesis RTL Schematic:

 

 **FULL SUBTRACTOR:**  
**Synthesis RTL Schematic:**



**Result:**

Thus the Adders and subtractors are simulated verified with VERILOG program.

**EX.NO:3**

**DATE:**

**CODE CONVERTERS-BINARY TO GRAY AND GRAY TO BINARY**

**Aim:**

To Simulate and synthesis Code converters- Binary to Gray and Gray to Binary using Verilog HDL

**Software tools required:**

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

**a) Binary to Gray and Gray to Binary**

**ALGORITHM:**

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using VERILOG source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.

**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

**Verilog Code for Binary to Gray code conversion:**

```
module bin2gray
    (input [3:0] bin, //binary input
     output [3:0] G //gray code output);
    //xor gates.
    assign G[3] = bin[3];
    assign G[2] = bin[3] ^ bin[2];
    assign G[1] = bin[2] ^ bin[1];
    assign G[0] = bin[1] ^ bin[0];
endmodule
```

**Verilog Code for Gray code to Binary conversion:**

```
module gray2bin
    (input [3:0] G, //gray code output
     output [3:0] bin //binary input );
    assign bin[3] = G[3];
    assign bin[2] = G[3] ^ G[2];
    assign bin[1] = G[3] ^ G[2] ^ G[1];
    assign bin[0] = G[3] ^ G[2] ^ G[1] ^ G[0];
endmodule
```

**Result:**

Thus the Binary to Gray and Gray to Binary are simulated verified with VERILOG program.

**EX.NO:4**

**DATE:**

### **3 TO 8 DECODER & ENCODER**

**Aim:**

To develop the source code for Decoder & Encoder by using VERILOG and obtain the simulation, synthesis, place and route and implement into FPGA.

**Software tools required:**

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

**DECODER & ENCODER:**

**Algoritm:**

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using VHDL source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.

**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

**PROGRAM:**

```
module Decoder(a,b,c,d0,d1,d2,d3,d4,d5,d6,d7);
```

```
input a,b,c;
```

```
output d0,d1,d2,d3,d4,d5,d6,d7;
```

```
assign d0=(~a&~b&~c),
```

```
d1=(~a&~b&c),
```

```
d2=(~a&b&~c),
```

```
d3=(~a&b&c),
```

```
d4=(a&~b&~c),
```

```
d5=(a&~b&c),
```

```
d6=(a&b&~c),
```

```
d7=(a&b&c);
```


```
endmodule
```

**DECODERS:**

Logic Diagram:

Truth Table

A	B	C	Z(0)	Z(1)	Z(2)	Z(3)
0	0	1	1	0	0	0
0	1	1	0	1	0	0

 

1	0	1	0	0	1	0
1	1	1	0	0	0	1

### **ENCODER:**

```

module encoder(D, x,y,z);
input [7:0] D;
output x,y,z;
assign x=D[4]|D[5]|D[6]|D[7];
assign y=D[2]|D[3]|D[6]|D[7];
assign z=D[1]|D[3]|D[5]|D[7];
endmodule

```

### **DECODER:**

#### **Behavioral-module**

```

module decoder(A,B,C,Z);
input A,B,C;
output [3:0] Z;
reg [3:0] Z;
reg xbar,ybar,zbar;
always @ (A or B ) begin
Abar=~A;
Bbar=~B;
Z[0]=Abar&Bbar&C;
Z[1]=Abar&B&C;
Z[2]=A&Bbar&C;
Z[3]=A&B&C;
end
endmodule

```

### **Result:**

Thus the Decoder & Encoder are simulated and verified with VERILOG program.

EX.NO:5

DATE:

### 4 BIT COMPARATOR

To develop the source code for 4 Bit Comparator by using VERILOG and obtain the simulation, synthesis, place and route and implement into FPGA.

#### Software tools required:

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

#### 4 BIT COMPARATOR:

##### Aloritm:

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using VHDL source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.

**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

#### 4 bit Comparator:

```
//declare the Verilog module - The inputs and output signals.
module comparator(
    Data_in_A, //input A
    Data_in_B, //input B
    less, //high when A is less than B
    equal, //high when A is equal to B
    greater //high when A is greater than B
);

//what are the input ports.
input [3:0] Data_in_A;
input [3:0] Data_in_B;
//What are the output ports.
output less;
output equal;
output greater;
//Internal variables
reg less;
reg equal;
reg greater;

//When the inputs and A or B are changed execute this block
always @(Data_in_A or Data_in_B)
begin
    if(Data_in_A > Data_in_B) begin //check if A is bigger than B.
        less = 0;
        equal = 0;
        greater = 1; end
    else if(Data_in_A == Data_in_B) begin //Check if A is equal to B
        less = 0;
        equal = 1;
        greater = 0; end
    else begin //Otherwise - check for A less than B.
```

```
        less = 1;  
        equal = 0;  
        greater = 0;  
    end  
end  
endmodule
```

**Result:**

Thus the 4 Bit Comparator is simulated and verified with VERILOG program.

EX.NO:6

DATE:

## 8 X 1 MULTIPLEXER & 1X4 DEMULTIPLEXER

### Aim:

To develop the source code for Multiplexer and Demultiplexer by using VERILOG and obtain the simulation, synthesis, place and route and implement into FPGA.

### Software tools required:

Synthesis tool: Xilinx ISE 8.2

Simulation tool: Project Navigator

### MULTIPLEXER AND DEMULTIPLEXER:

#### Aloritm:

**Step1:** Define the specifications and initialize the design.

**Step2:** Declare the name of the entity and architecture by using VHDL source code.

**Step3:** Write the source code in VERILOG.

**Step4:** Check the syntax and debug the errors if found, obtain the synthesis report.


**Step5:** Verify the output by simulating the source code.

**Step6:** Write all possible combinations of input using the test bench.

**Step7:** Obtain the place and route report.

### MULUTIPLEXER:

#### Logic diagram:

 

#### Truth table:

INPUT		OUTPUT
s[1]	s[0]	y
0	0	D[0]
0	1	D[1]
1	0	D[2]
1	1	D[3]

### VERILOG SOURCE CODE:

#### Dataflow Modeling:

```
module muxdataflow(s, i, y);  
    input [1:0]s;  
    input [3:0]i;  
    output y;  
    wire f1,f2,f3,f4,f5,f6;  
    assign f1=~s[1];  
    assign f2=~s[0];
```



```

        assign f3=i[0]&f1&f2;
        assign f4=i[1]&f1&s[0];
        assign f5=i[2]&s[1]&s[0];
        assign f6=i[3]&s[1]&s[0];
        assign y=f3|f4|f5|f6;
    endmodule

    module Mux(d0,d1,d2,d3,d4,d5,d6,d7,sel,out);
    input d0,d1,d2,d3,d4,d5,d6,d7;
    input [2:0] sel;
    output reg out;
    always@(sel)
    begin
        case(sel)
            3'b000:out=d0;
            3'b001:out=d1;
            3'b010:out=d2;
            3'b011:out=d3;
            3'b100:out=d4;
            3'b101:out=d5;
            3'b110:out=d6;
            3'b111:out=d7;
        endcase
    end
    endmodule

```

### Simulation output:




### Synthesis RTL Schematic:



### DEMULTIPLEXER: LOGIC DIAGRAM:

### Truth table:

INPUT			OUTPUT			
D	S0	S1	Y0	Y1	Y2	Y3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

### **VERILOG SOURCE CODE:**


#### **Dataflow Modeling:**

```


module demuxdataflow((din, s0, s1, d);
    input din;
    input s0;
    input s1;
    output [3:0]d;
    wire f1,f2;
    assign f1=~s1;
    assign f2=~s0;
    assign d[0]=din&f1&f2;
    assign d[1]=din&f1&s0;
    assign d[2]=din&s1&f2;
    assign d[3]=din&s1&s0;
endmodule

```

#### **Simulation output:**

 

#### **Synthesis RTL Schematic:**

 

### **RESULT:**

Thus the output's of 8 X 1 MULTIPLEXER & 1X4 DEMULTIPLEXER are verified by synthesizing and simulating the VERILOG code.

EXP NO: 07

DATE:

## DESIGN OF FILP-FLOPS USING VERILOG HDL IN XILINX PLATFORM

### **Aim:**

To develop the source code for flip-flops by using VERILOG and obtain the simulation.

### **Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

### **Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using VERILOG source code.


Step3: Write the source code in VERILOG.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

### **SR Flip Flop:**

#### **Logic Diagram:**

 


#### **Truth Table:**

Q(t)	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	x

### **SR Flip Flop - Program:**

```
module srff_clk(s, r, clk, q, qn);
input s, r, clk, q;
output qn;
reg qn;
always @(posedge clk,s,r,q)begin
qn=(s|((~r)&q));
end
endmodule
```


### **Simulation Output:**

 

### **Schematic Diagram:**

### **D Flip Flop:**

Logic Diagram:

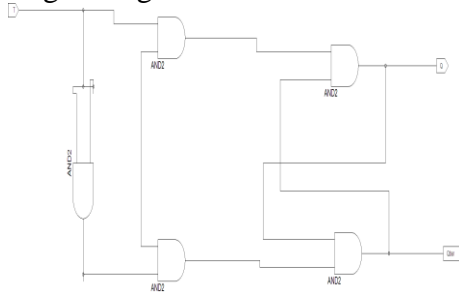

Truth Table:

Q(t)	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

### **Program:**


```
module DFF(d, clk, q);
input d;
input clk;
output q;
reg q;
always @(posedge clk)begin
q=d;
end
endmodule
```

### **Simulation Output:**

### **RTL Schematic:**




### **Schematic Diagram:**

 

### **T- Flip Flop:**

Logic Diagram:

 

Truth Table:

Q(t)	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

### **Program:**


```
module TFF(t, clk, q,qout);
input t,q;
input clk;
output qout;
reg qout;
always @(posedge clk)begin
qout=t^q;
end
endmodule
```

### **Simulation Output:**


### RTL Schematic:



### Schematic Diagram:

 


### Schematic Diagram:

 

### JK Flip Flop:

#### Logic Diagram:

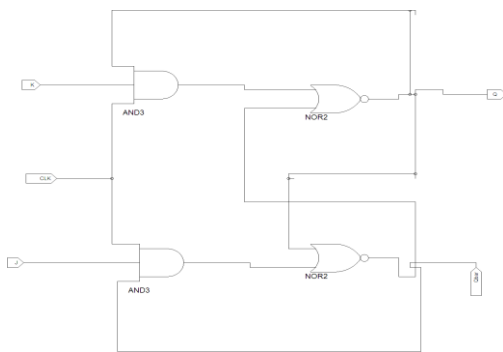


#### Truth Table:

Q(t)	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

### Program:

```
module JKFF(J,K, clk, q,qout);
input J,K,q;
input clk;
output qout;
reg qout;
always @(posedge J,K,q, clk)begin
qout=(J&(~q))|(q&(~K));
end
endmodule
```

### Schematic Diagram:

 

### Simulation Output:

**Result:** Thus, the flip flops (SRFF,DFF,TFF,JKFF) are simulated and synthesized with verilog program.

**EXP NO: 08**

**DATE:**

**DESIGN OF COUNTER USING VERILOG HDL IN XILINX PLATFORM**

**Aim:**

To develop the source code for counter by using VERILOG and obtain the simulation.

**Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

**Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using VERILOG source code.

Step3: Write the source code in VERILOG.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

**Verilog Code:**

**I. Up Counter:**

```
module upcounter (out, enable, clk, reset);
output [7:0] out;
input enable, clk, reset;
reg [7:0] out;
always @(posedge clk)
if (reset) begin
out <= 8'b0 ;
end else if (enable) begin
out <= out + 1;
end
endmodule
```


**II. Up Down Counter:**

**Program:**


```
module up_down_counter (out , up_down
,clk ,reset );
output [7:0] out; input up_down, clk, reset;
reg [7:0] out;
always @(posedge clk)
if (reset) begin
out <= 8'b0 ;
end else if (up_down) begin
out <= out + 1;
end else begin
out <= out - 1;
end
end
endmodule
```

**Simulation Output:**

**RTL Schematic:**

 

**Schematic Diagram:**

 

**Result:**

Thus the various counters are simulated and synthesized with verilog program.

**Exp No: 09**

**Date:**

## **4 BIT UP COUNTER WITH ASYNCHRONOUS**

### **AIM:**

To develop the source code for 4 BIT UP COUNTER with Asynchronous generator by using verilog and obtain the simulation.

### **Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

### **Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using verilog source code.

Step3: Write the source code in verilog.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

## **Asynchronous Counter:**

### **4-bit Unsigned Up Counter with Asynchronous**

```
module counter (C, CLR, Q);
input C, CLR;
output [3:0] Q;
reg [3:0] tmp;
always @(posedge C or posedge CLR)
begin
if (CLR)
tmp = 4'b0000;
else
tmp = tmp + 1'b1;
end
assign Q = tmp;
endmodule
```

### **4-bit Unsigned Down Counter with Synchronous:**

```
module counter (C, S, Q);
input C, S;
output [3:0] Q;
reg [3:0] tmp;
always @(posedge C)
begin
if (S)
tmp = 4'b1111;
else
tmp = tmp - 1'b1;
end
assign Q = tmp;
endmodule
```

### **Result:**

Thus the 4 bit and 8 bit PRBS generator is simulated and synthesized with verilog program.

**SHIFT REGISTER****Aim:**

To develop the source code for Shift Register by using verilog and obtain the simulation.

**Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

**Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using verilog source code.

Step3: Write the source code in verilog.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

**SHIFT REGISTER:**

```
module shift_register(s1,d,clk,s0,q);
  parameter n=3;
  input s1,clk;
  input [n:0] d;
  output s0;
  output [n:0] q;
  genvar i;
  assign d[3]=s1;
  generate
  for(i=0; i<=n; i=i+1)
    dff U1(.d(d[i]),.q(q[i]),.clk(clk));
  endgenerate

  assign q[3]=d[2];
  assign q[2]=d[1];
  assign q[1]=d[0];
  assign q[0]=s0;
endmodule
```

**Result:**

Thus the Shift Register is simulated and synthesized with verilog program.



**DESIGN OF ACCUMULATOR USING VERILOG HDL IN XILINX PLATFORM****Aim:**

To develop the source code for accumulator by using verilog and obtain the simulation.

**Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

**Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using verilog source code.


Step3: Write the source code in verilog.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

**Program:**

```
module accum (C, CLR, D, Q);
input C, CLR;
input [3:0] D;
output [3:0] Q;
reg [3:0] tmp;
always @(posedge C or posedge CLR)
begin
    if (CLR)
        tmp = 4'b0000;
    else
        tmp = tmp + D;
    end
    assign Q = tmp;
endmodule
```

 **Simulation Output:****RTL Schematic:****Schematic Diagram:****Result:**

Thus the accumulator is simulated and synthesized with verilog program.

**EXP NO: 12**

**DATE:**

**DESIGN OF ARITHMETIC LOGIC UNIT USING VERILOG HDL IN XILINX  
PLATFORM**

**Aim:**

To develop the source code for arithmetic logic unit by using verilog and obtain the simulation.

**Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

**Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using verilog source code.

Step3: Write the source code in verilog.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

**Program:**

**Simulation Output:**

```
module alu(out, a,b, opcode);
output [7:0] out;
input [3:0] a,b;
input [1:0] opcode;
reg [7:0]out;
parameter
ADD=2'b00,
SUB=2'b01,
MUL=2'b10,
DIV=2'b11;
always @(a,b,opcode)
case(opcode)
ADD:out=a+b;
SUB:out=a-b;
MUL:out=a*b;
DIV:out=a/b;
endcase
endmodule
```

**Result:**

Thus the arithmetic logic unit is simulated and synthesized with verilog program.

### **Exp No: 13**

### **Date:**

## **DESIGN OF PRBS GENERATOR USING VERILOG HDL IN XILINX PLATFORM**

### **Aim:**

To develop the source code for PRBS generator by using verilog and obtain the simulation.

### **Software Required:**

- Xilinx – Project Navigator
- ModelSim Simulator

### **Procedure:**

Step1: Define the specifications and initialize the design.

Step2: Declare the name of the module by using verilog source code.

Step3: Write the source code in verilog.

Step4: Check the syntax and debug the errors if found, obtain the synthesis is report.

Step5: Verify the output by simulating the source code.

### **4-Bit PRBS Generator:**

#### **Program:**


```
module prbs(rand,clk,rst);
input rst,clk;
output [3:0]rand;
wire [3:0]rand;
reg [3:0]temp;
always @(posedge clk or posedge rst)
begin
if(rst)
begin
temp<=4'b1111;
end else
begin
temp<={ temp[0]^temp[1],temp[3],temp[2],temp[1]};
end end
assign rand=temp;
endmodule
```

### **8-Bit PRBS Generator:**


#### **Linear feedback shift register**

```
module lfsr (data, out, enable , clk , reset);
output [7:0]
input [7:0] data;
input enable, clk, reset;
reg [7:0] out;
wire linear_feedback;
assign linear_feedback = !(out[7] ^ out[3]);
always @(posedge clk)
if (reset) begin
out <= 8'b0 ;
end else if (enable) begin
out <= {out[6],out[5],
out[4],out[3],
out[2],out[1],
out[0], linear_feedback};
end
endmodule
```

### **RTL Schematic:**

 

### **Schematic Diagram:**

 

### **Result:**

Thus the 4 bit and 8 bit PRBS generator is simulated and synthesized with verilog program.

## **Exp No: 14**

### **Date:**

## **STUDY OF PLACE AND ROUTE AND BACK ANNOTATION FOR FPGA**

### **Aim:**

To study Place and Route and Back annotation for FPGA using Xilinx Project Navigator software.

### **Software Required:**


- Xilinx – Project Navigator.
- ModelSim Simulator.

### **Theory:**


Before timing simulation can occur, the physical design information must be translated and distributed back to the logical design. For FPGAs, this back-annotation process is done with a program called NetGen. For CPLDs, back-annotation is performed with the TSim Timing Simulator. NetGen distributes information about delays; setup and hold times, clock to out, and pulse widths found in the physical NCD design file back to the logical NGD file and generate a Verilog or VHDL netlist for use with supported timing simulation, equivalence checking, and static timing analysis tools.
 
### **Procedure:**

- Open Xilinx -> Project Navigator.
- Select File -> NEW PROJECT.





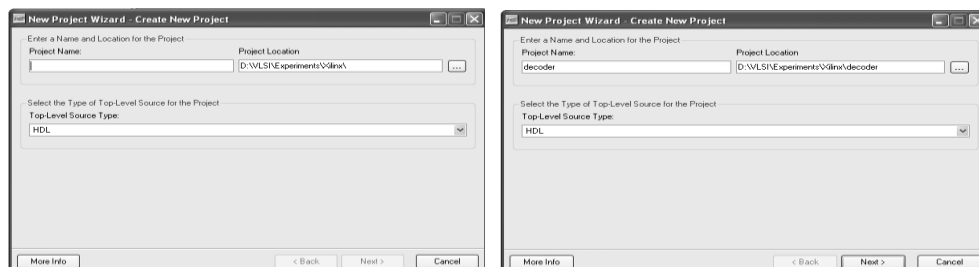- In the New Project Wizard, do the following:
  - In the Project Name field, enter a name for the project as decoder.
  - In the Project Location field, enter the directory name or browse to the directory.
  - In the Top-Level Module Type drop-down list, select HDL and click Next.






- In the Device Properties page of the New Project Wizard, set the following options.
  - Product Category – All
  - Family – Spartan3E
  - Device – XC3S500E
  - Package – FG320

 
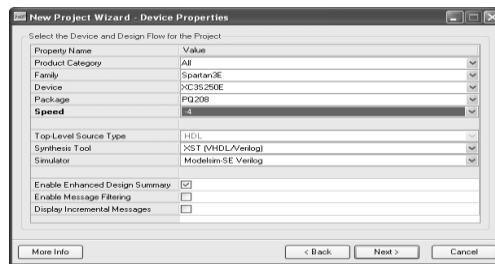
- Speed Grade – 4
- Verify that Enable Enhanced Design Summary is selected.



   - If you are creating an HDL or schematic project, click Next, and optionally, create a new source file for your project.
- Click New Source. Select Verilog Module in New Source Window and enter the File Name as decoder and click Next.
- Again click Next and click Finish.
- Click Next.




  - Click Next to display the Information page of the New Project Wizard and finally click finish to create the project.
- Double click the file name, which is inside the Sources in Project window and write the program for 3:8 Decoder using Verilog.




- Highlight the \*.v file in the Sources in Project window.
- Go to Processes for Source window.
- Double click Generate Post-Place & Route Simulation Model, which is inside Place and Route.
- After all the processes before Place and Route is over, the window looks as shown below.

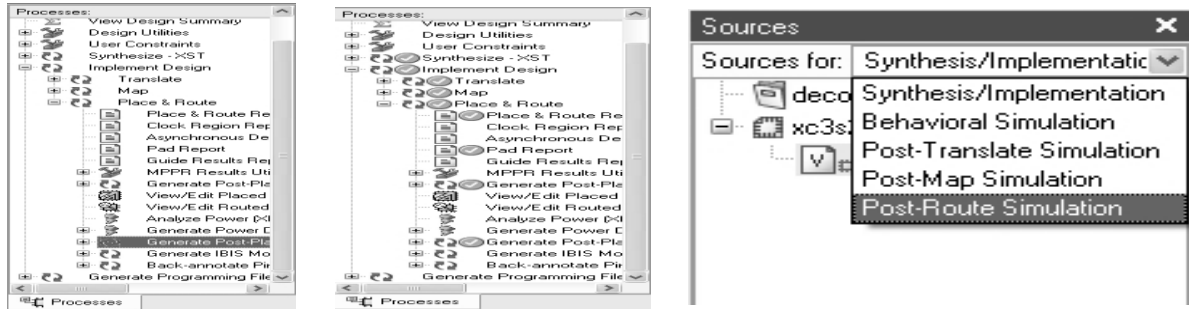
- Select Post-Route Simulation in Sources window.



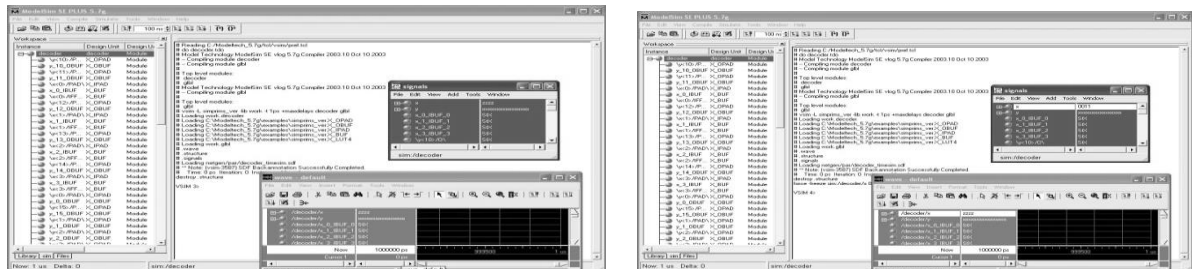- After you select the file name, Run Simulate Post-Place and Route Model in Processes Window.
- After you run the previous process, ModelSim Window is opened.
- Now Force signal “x” to “001” and click the Run button in Waveform Window
- Now you can see the output waveform including the gate delays and net delays



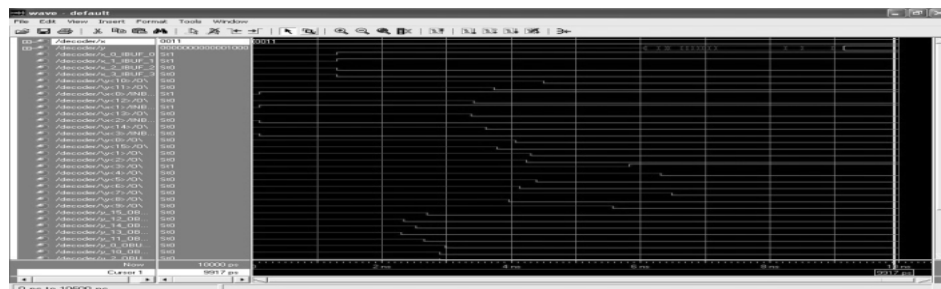- Thus by doing Post-Place and Route Simulation, we get the Back-Annotated waveform.



**Program of any Combinational Circuits:**

**Result:**

Thus we have studied the Place and Route and Back annotation for FPGA software.

Exp No: 15

Date:

## STUDY OF SYNTHESIS FOR XILINX TOOLS

### Aim:

To study the various synthesis tools used in the Xilinx - Project Navigator software using Full adder logic circuit as an example.

### Software Required:


- Xilinx – Project Navigator.

### Theory:


At the time when the development of VHDL was initiated the major concern was to have a standardized and unique method for documentation of complex digital circuits which would also allow simulating the circuit descriptions. Based on these objectives, VHDL provided semantic elements mainly for simulation purposes.. In the context of software tools and VHDL, synthesis is an automatic method of converting a higher level abstraction, such as a behavioral description, to a lower level abstraction, for example, a gate-level net list.
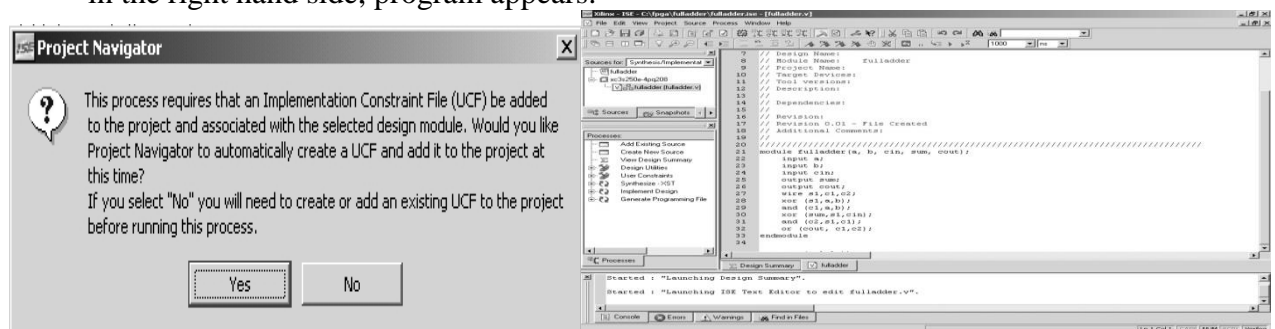
### Procedure:


- Now start the Project Navigator. The previous project appears. Select the Verilog module, in the right hand side, program appears.




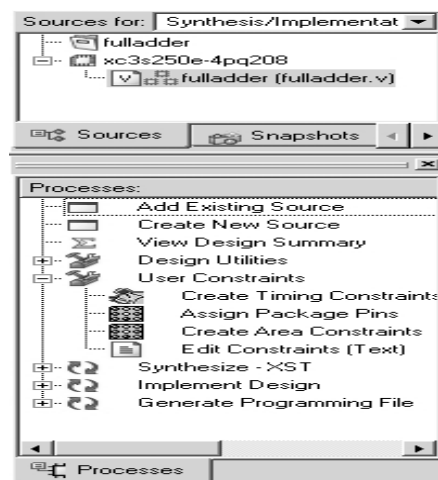
- In Sources window, select Synthesis/Implementation. In process, select + in User Constraints.



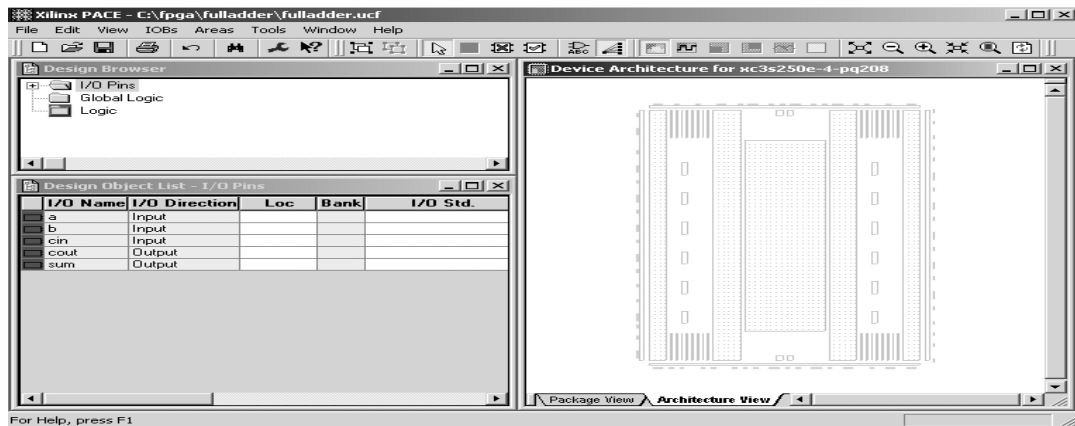
- Select Assign Package Pins. It gives message that User Constraint File will be created. Click Yes.
- Xilinx PACE Software window appears with I/O names. Select Loc.



 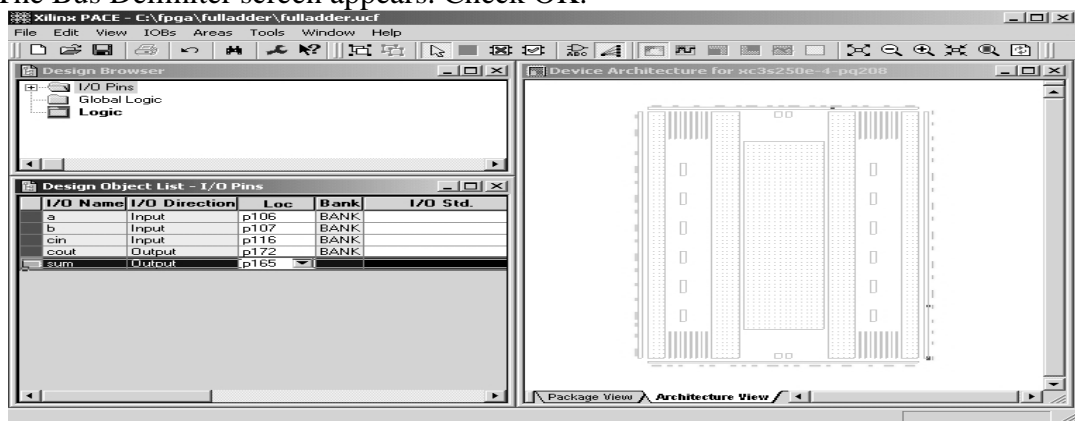- Give Pin numbers say for signal a, 113. In our FPGA Kit, 113 is connected to DIP switch.
- Select input pins from switches and output pins from LED bar graph and then save.
- The Bus Delimiter screen appears. Check OK.






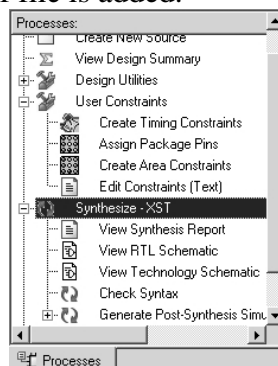
- Then exit from the Xilinx PACE window.
- In the main window, fulladder.ucf file is added.




- Click the verilog module. In Processes window, Synthesis, Implement design and Generate Programming file appears.
- Select + in Synthesis.



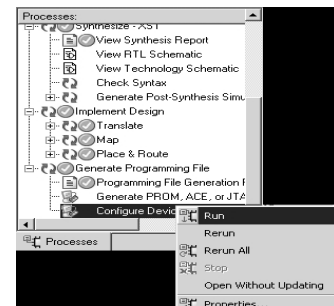  
 
- Select Synthesis and right click and Run.
- After completing the synthesis, a tick mark appears
- Then select + in Implement design and select it. Right click and Run.
- It will run the following : Translate, Map, Place and Route functions
- Then select + in Generate Programming Files and generate it by right clicking and select Run.






 
- After generating the Programming file, select Configure Device (IMPACT) and right click and Run.
- Xilinx IMPACT software is opened and welcome screen appears.



  
- Select Prepare a PROM File and then next.




- In this next screen, select Xilinx PROM and PROM file format MCS. In our FPGA Kit, Xilinx PROM is used to store the program for FPGA and the PROM file format is MCS.
- In the next screen, the particular Xilinx PROM is selected
- In our Kit, xcf04s Platform Flash PROM is present and this device is chosen.
- Then click Add button is pressed to select this PROM.
- In the next screen, the file generation summary is given.
- 

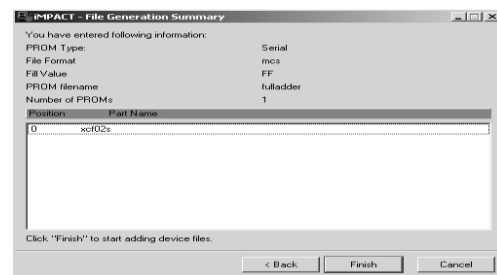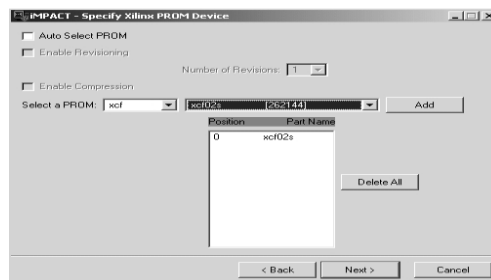  

 
- In the next screen, diagram of Xilinx PROM appears. In this screen, click OK.



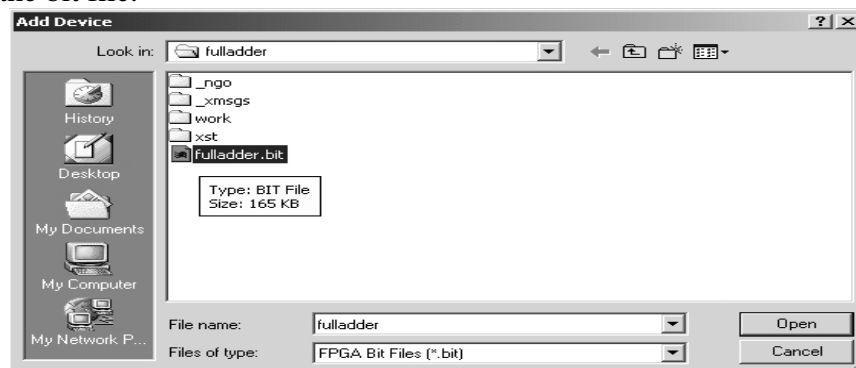
- The generated bit file is used to generate the PROM file in the MCS format. The next screen displays the bit file.



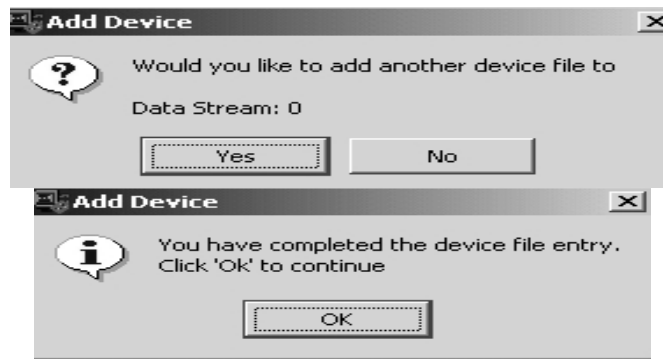
- When it asks for adding of additional device, click NO.
- Click OK in the next window when it asks for continuation.




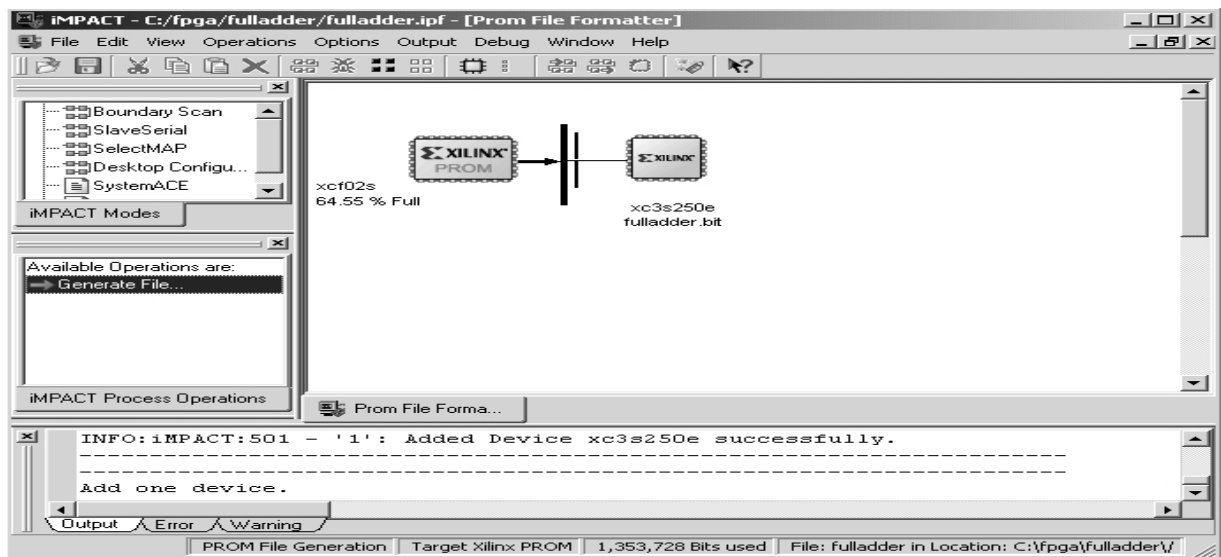
- Click Generate file in the available operations and the PROM file is generated and it is indicated in the screen.



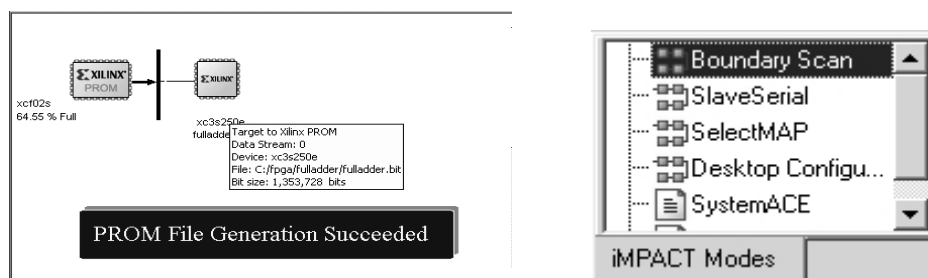
- Switch on the Kit which is connected to the Parallel port of the system. Double click Boundary Scan in the iMPACT modes. During Boundary scan, the kit should be ON.



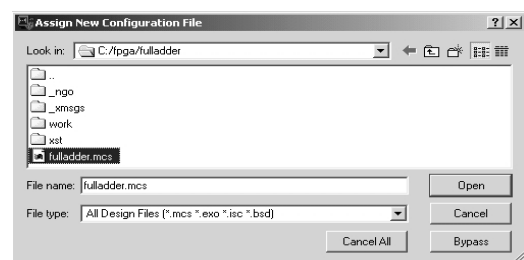 
- In the right hand side, plain window appears. Right click in this window and select Initialize chain.



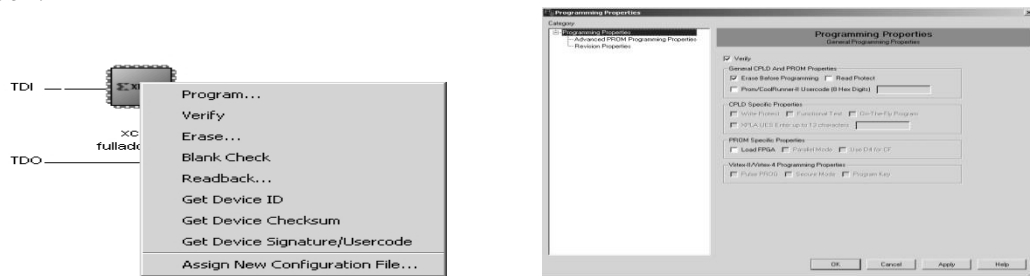- Next, a window appears with generated PROM file. Select the MCS format file and click Open.



 - Now, that file has been taken for programming. Keep the cursor on the device and right click.



- Select the Program .Programming Properties screen appears. Select verify and erase before programming.
- Once you click OK, the program is downloaded to the PROM.
- Finally, the “Program succeeded” screen appears.
- In the kit, press the Prog key. Now, the program in the PROM is loaded to the FPGA and the FPGA acts according to the circuit designed.

### Result:

Thus the study about various synthesis tools used in the Xilinx - Project Navigator software is studied.